

6/12/19

# Basics of Electronics

(i) ~~Diode~~ R, C, L, Diode &

Transistor

BJT

MOSFET

## Basic Properties of Resistor (R)

- It opposes current flow. It is a protective element.

~~to limit maximum current~~  
~~use positive voltage across it~~  
~~resistance =  $\frac{V}{I}$~~   
~~if  $V=0$ , then  $I=\infty$~~   
 ~~$\frac{V}{0} = \infty$  resistance~~

$$5V \xrightarrow{R} 0V$$

$$5V \xrightarrow{R} 5mA$$

~~current flow depends on voltage of source, or resistor value.~~

- Voltage source in series with a resistor acts as current source.

Resistor + Voltage source  $\rightarrow$  current source


$$= \frac{1}{R} \propto V \quad (V \propto I \propto V/R)$$

current source. (get collector current)



3.

## Scaling Resistance

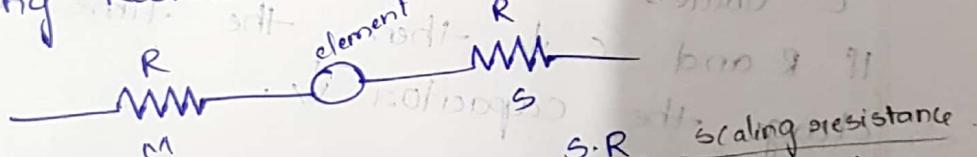

parallel

control


base 2

scaling resistance


 $\frac{S.R}{M.R}$  Main resistance

$$\text{Scaling factor} = \text{Gain} = \frac{S.R}{M.R}$$


## 4. Phase splitting

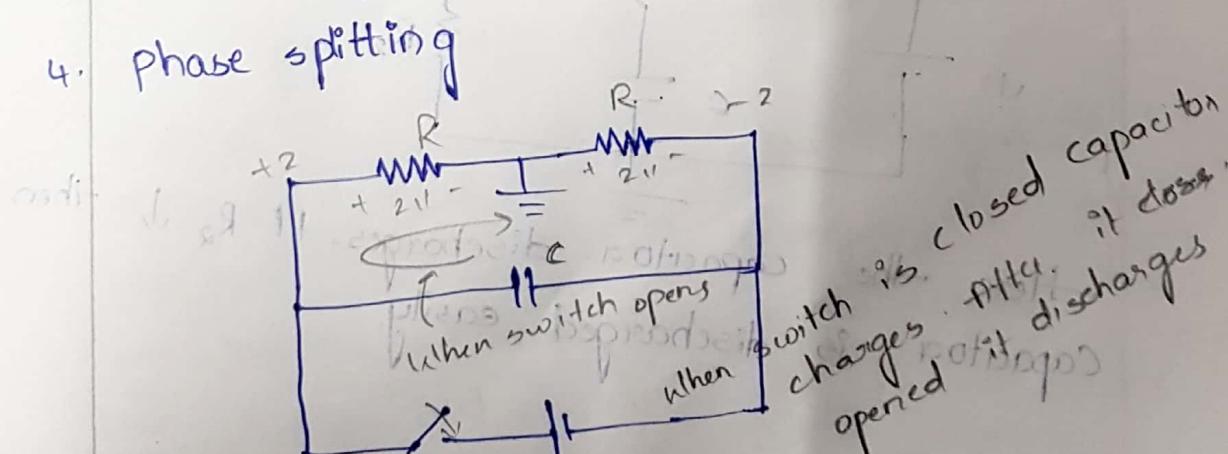

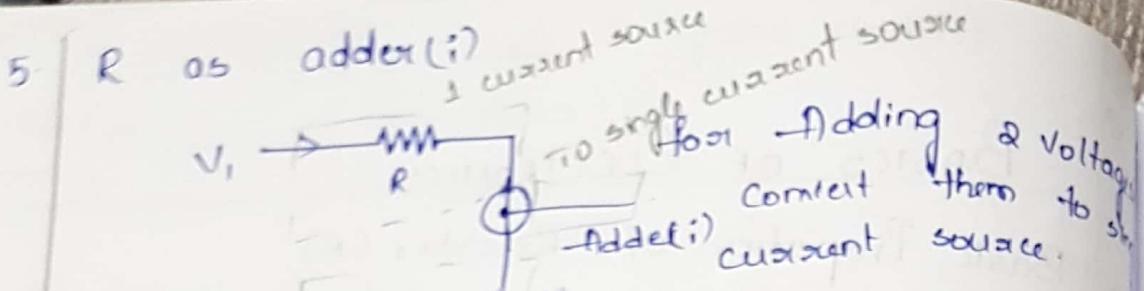
closed capacitor  
 When switch opens, it does not discharge  
 When switch closes, it charges after opening



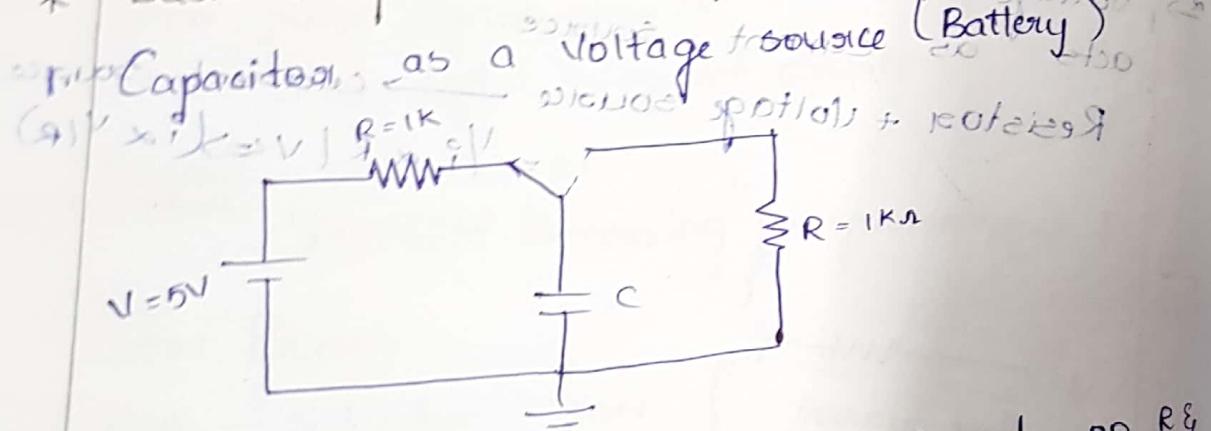- \* Note: 1st is 1st current source & 2nd is 2nd current source.
- Voltage to current converter / is resistor that is the 1st resistor in series with voltage source to get current source.
- Resistor is also current to voltage converter.
- \* Basic Properties of Capacitor (C)




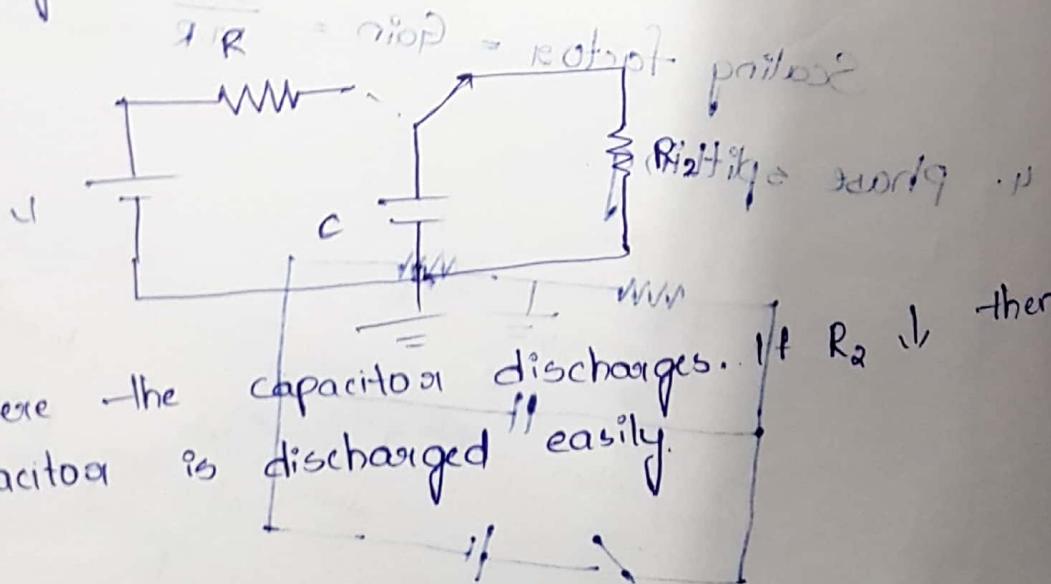charging of the capacitor depends on R & C values. If R and C are then the time taken to charge the capacitor.



Here the capacitor discharges. If  $R_2 \downarrow$  then capacitor is discharged easily.

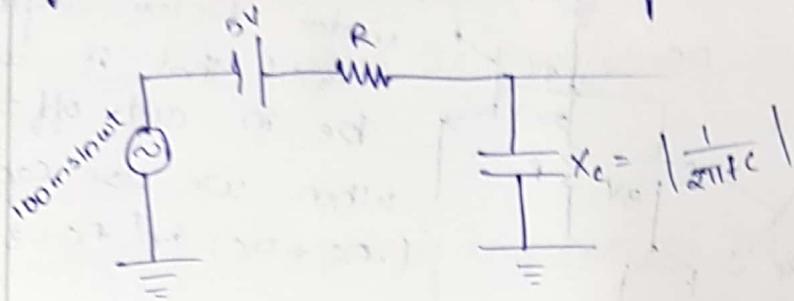2. Capacitor as a filter.  
If C value is more then capacitor can ground the low frequency ripples also




$$i = C \frac{dv}{dt} \text{ at sudden change } dt=0 \Rightarrow i = \infty$$

so capacitor is short circuit.

so capacitor acts as a phase splitter.

3. Capacitor as a tank circuit


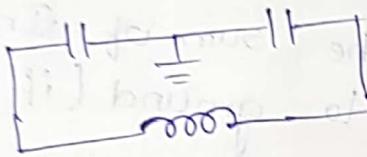


4. Capacitor as a adder

When S is connected

to ground,

is given to capacitor  
so it charges.

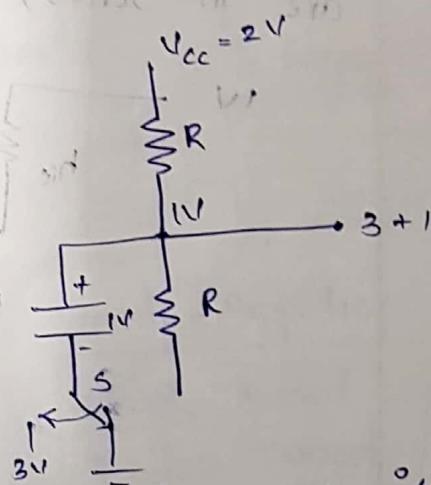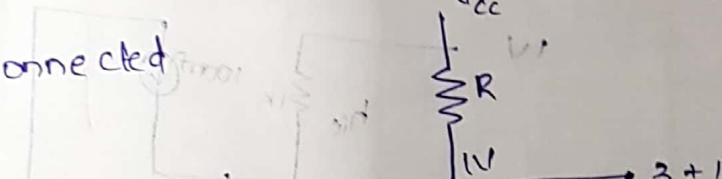

When S is moved to 3V then 3V is given to capacitor so total of (3+1) V we get at o/p so capacitor acts as

Adder.


Before

$t=1$  sec capacitor charged to 1V

After

$t=1$  sec it charges to 3V

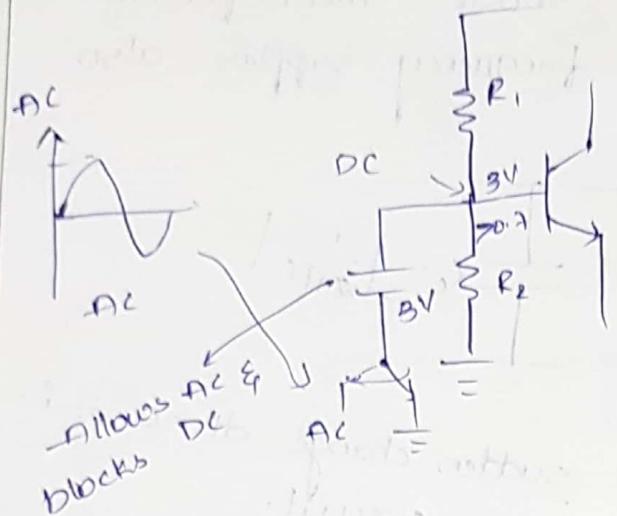In Amplifier circuit capacitor acts as both adder and filter.




$\rightarrow 0.4V$  is only the voltage across  $R_1$  under active region until that it will be in cut off region when we use capacitors  $(-AC + DC) \text{ rel } AC + 3$
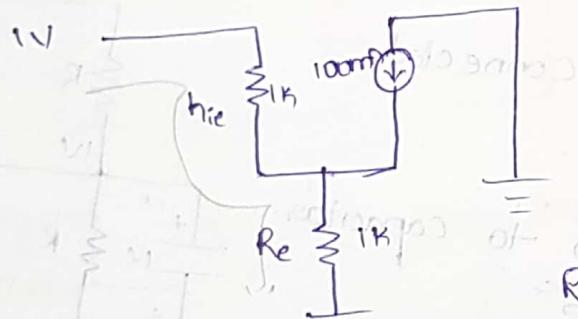
## 6. Basic Resistor properties

\* Calculation of Thévenin resistance for any circuit

Total resistance across the branch from 1 node to ground is the sum of individual resistances from that node to ground (if those resistances are in series)



When we want to find resistance b/w 1V & ground

$h_{ie}$  &  $R_e$  must be series so changing  $R_e$  to 100k results in the flow of 1mA current same as in  $h_{ie}$

$$\text{Total resistance} = 2k + 100k = 102k$$

also, ratio of comp

of bipots ratios  $\frac{R_{max}}{R_{min}}$

of bipots  $\frac{100k}{2k} \times \frac{100k}{100k} = 50$

$R_{max} = 100k$


$R_{min} = 2k$

11/19

## UNIT-1: Frequency Response of BJT Amplifier


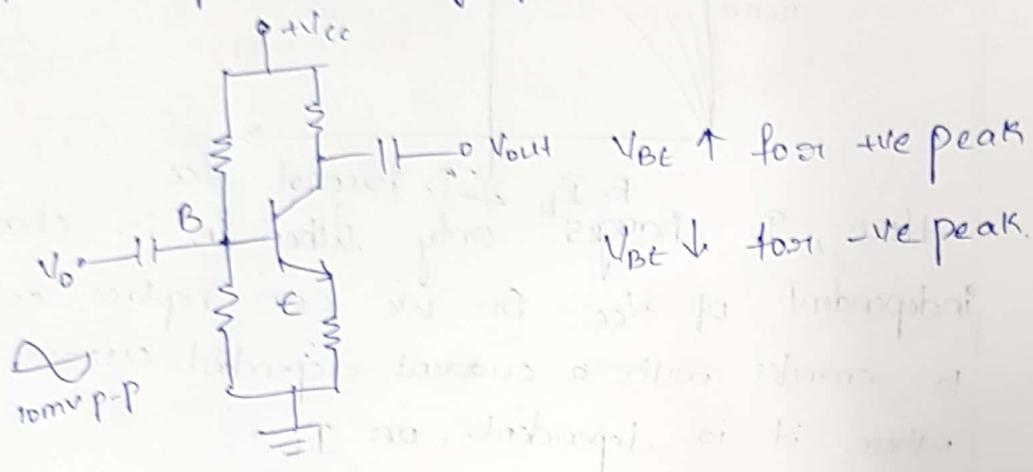
### a. Hybrid $\pi$ -model.

for any small signal amplifier when we give some voltage then  $V_{BE}$  slightly increases for positive peak & slightly decreases for negative peak.


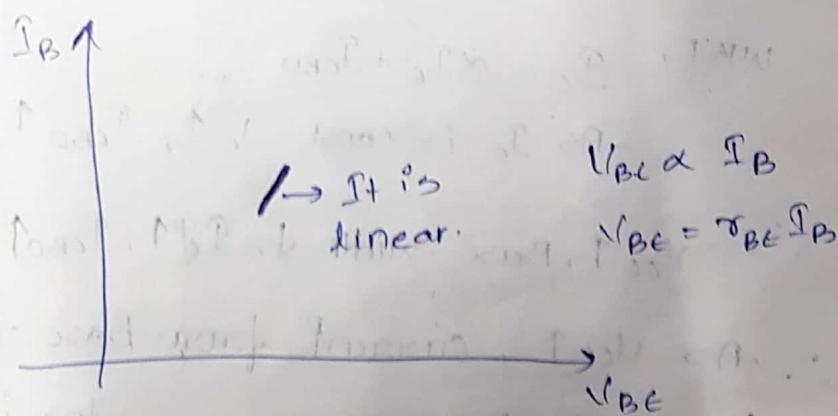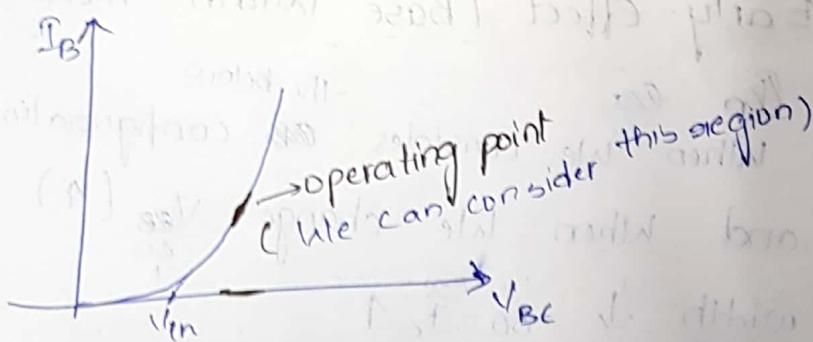
### 1. Input characteristics


for doing analysis, we must have a linear element but the transistor is non linear so to make it linear we replace it with different linear models like  $\pi$ ,  $h$  &  $\gamma$ .




Here we replace a resistor  $R_{BE}$  across Base

emitter or at i/p

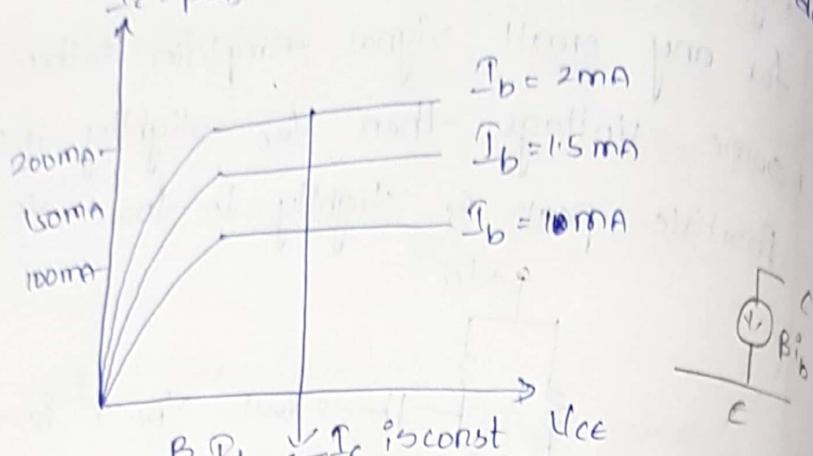$I_c = \beta I_B \rightarrow$  current controlled current source



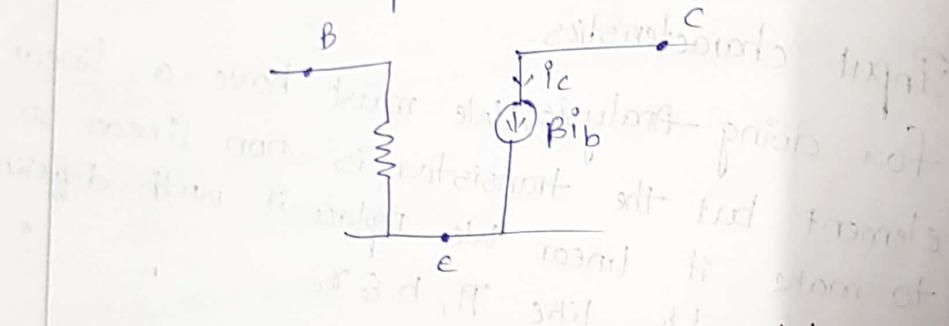Here,  $I_c$  changes only when  $I_b$  is changed independent of  $V_{CE}$ . So we can replace collector to emitter with a current dependent current source where it is dependent on  $I_b$ .



### 3. Early Effect / Base width modulation



In ex. when we consider  $\text{C-E}$  configuration,  $V_{BE}$  is const and when we change  $V_{CE}$  ( $\uparrow$ ) then Base width  $\downarrow$  so  $I_c \uparrow$

$$\text{WKT}, \quad I_c = \alpha I_e + I_{CB0}$$




As  $I_e$  is const  $I_c \uparrow, I_{CB0} \uparrow$

$\therefore V_{CE} \uparrow, \text{Base width} \downarrow, I_c \uparrow, I_{CB0} \uparrow$

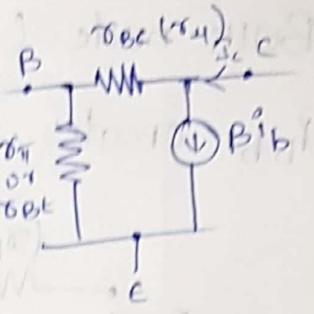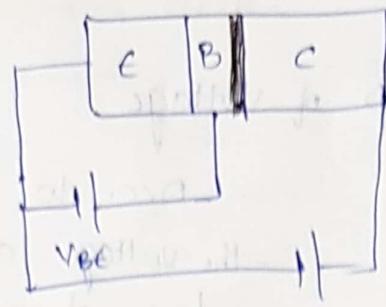$\therefore$  As  $V_{CE} \uparrow$ , current from Base to current ( $I_{BE}$ )  $\uparrow$  so we can keep a resistor in b/w C & B



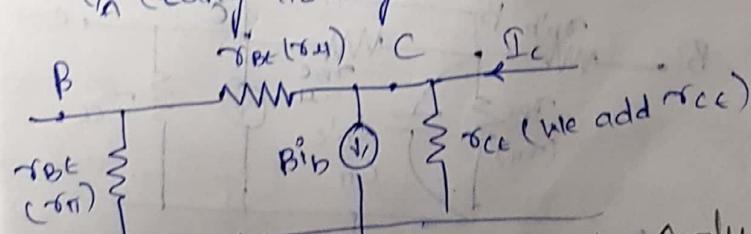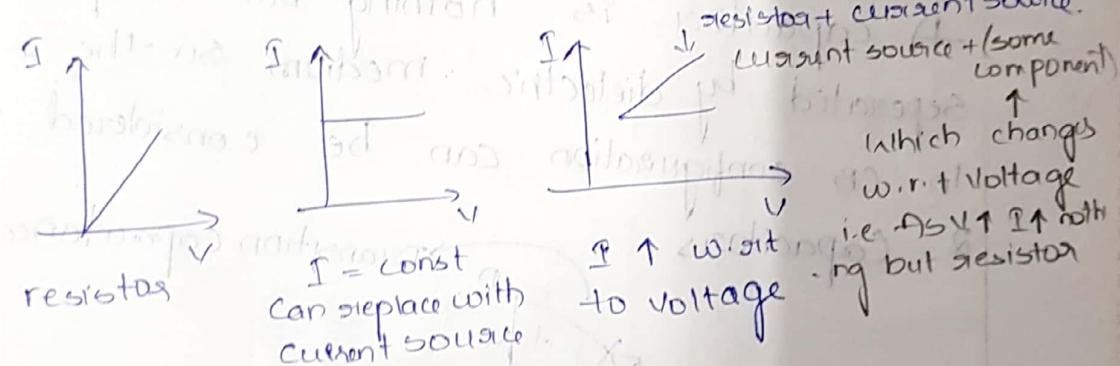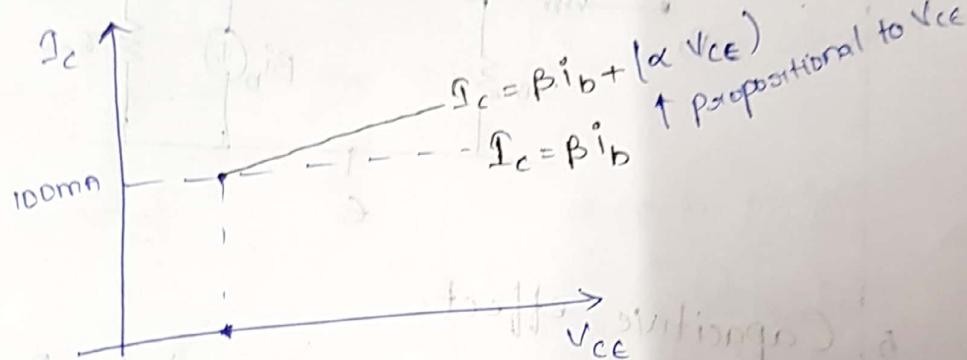
Generally acc. to D/p characteristics  $I_c$  is const.  
though  $V_{ce}$  ↑, But acc. to early effect  $I_c$  ↑  
when  $V_{ce}$  is ↑ so the D/p characteristics  
should be modified.




We add  $r_{BE}$  &  $r_{CE}$  due to early effect

#### 4 Bulk node ( $B'$ )

$r_{bb'}$  creates a drop of voltage

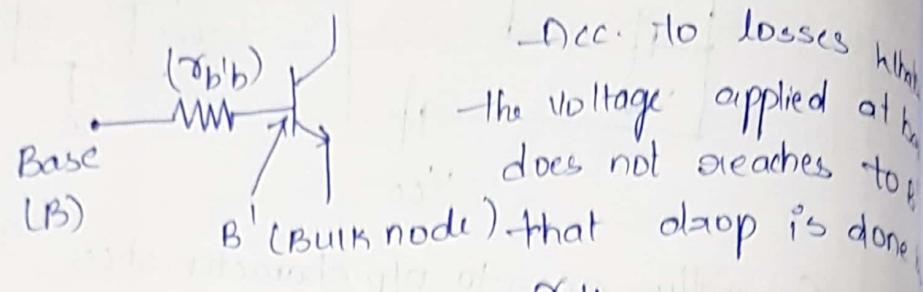


$r_{bb'}$  - Base spreading resistor.

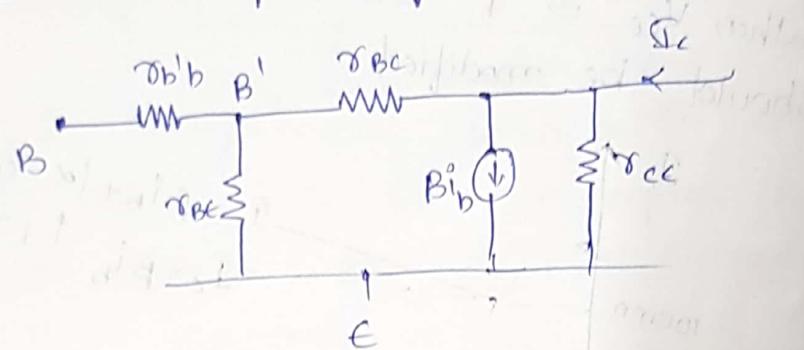


#### 5. Capacitive effect.

A capacitor is nothing but 2 parallel plates separated by dielectric medium so the 2 junctions in CB configuration can be considered as


##### 2 Capacitors

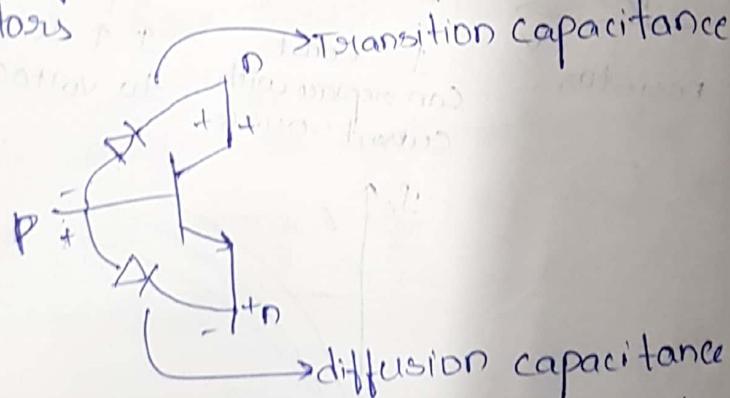

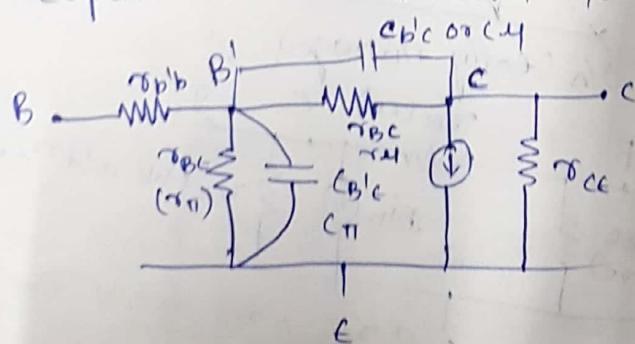
So capacitors are connected b/w  $B'$  &  $C$ ,  $B'$  &  $E$



## B. h-parameter model.

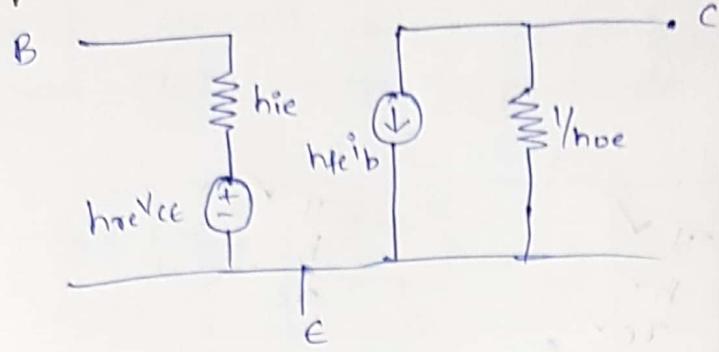


Approximation:

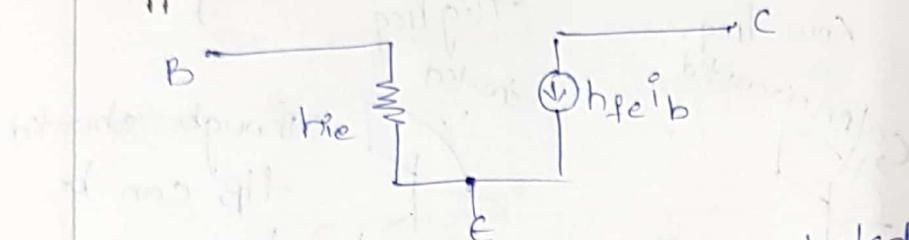


Here capacitive effect is neglected so it fails in many cases so we consider tr-model.

## C. $\pi$ -model.

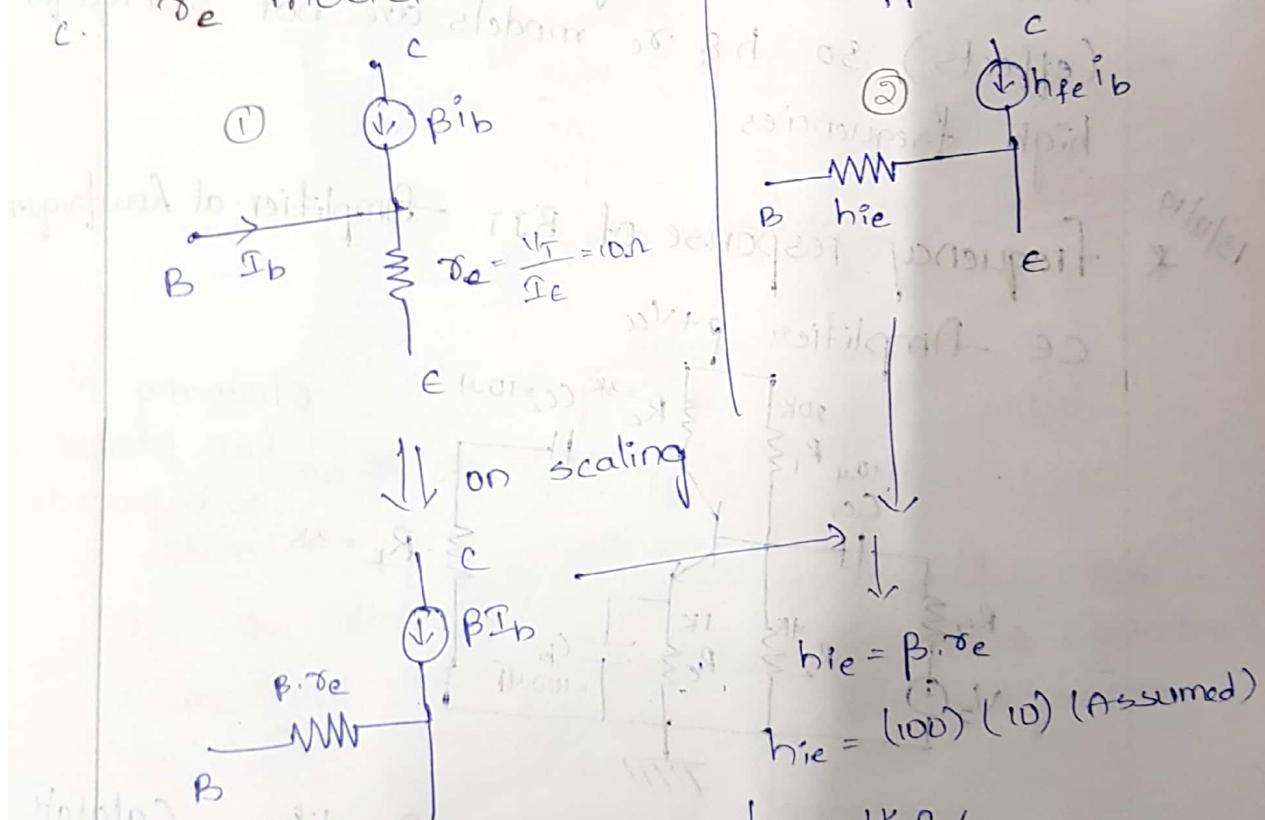

① Here base current & constant collector current is limited at emitter by  $\pi_e$

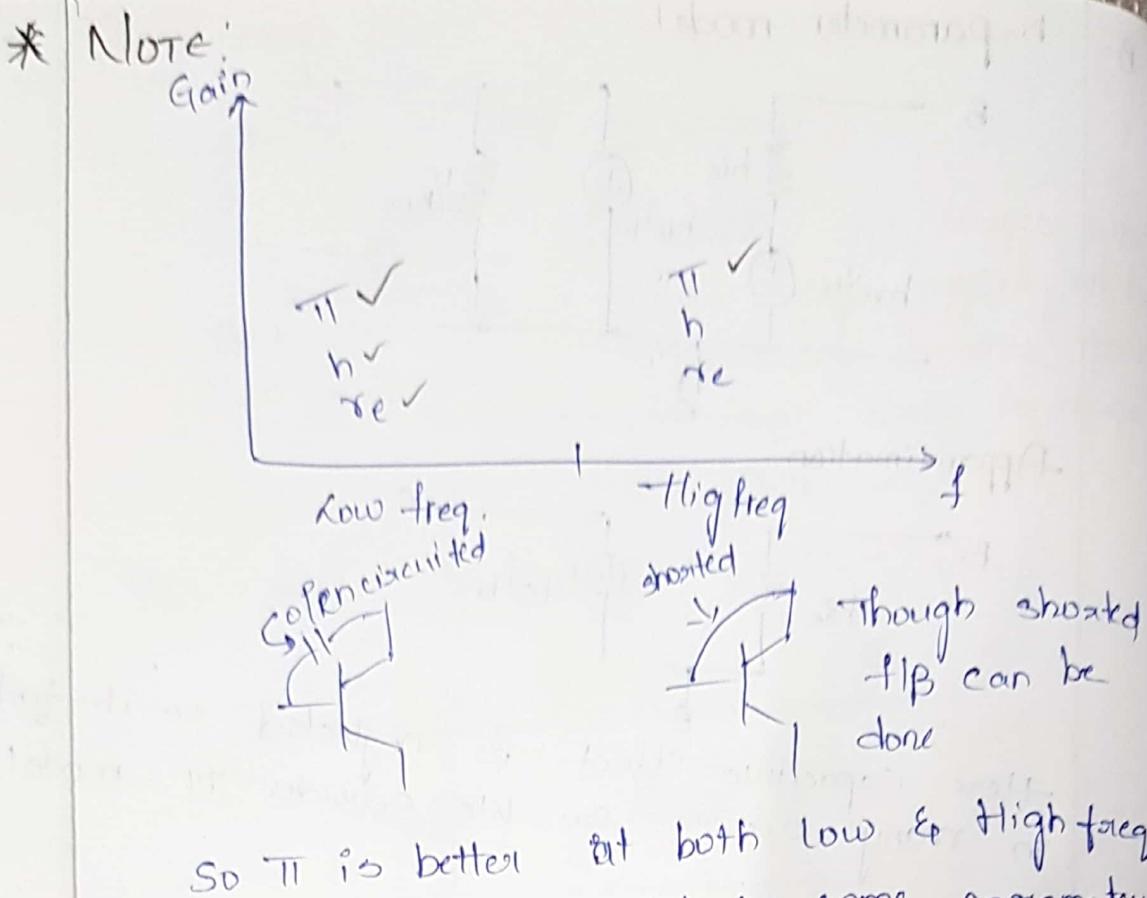
② Electron current from base is limited by  $hie$  so collector current also when it enters to emitter.



So  $\pi$  is better at both low & high freq.  
but  $h$  &  $re$  are neglected by some parameters  
(effects) so  $h$  &  $re$  models are not suited for  
high frequencies

13/12/19 \* frequency response of BJT - Amplifier at low frequency

ce - Amplifier  $p+V_{CC}$

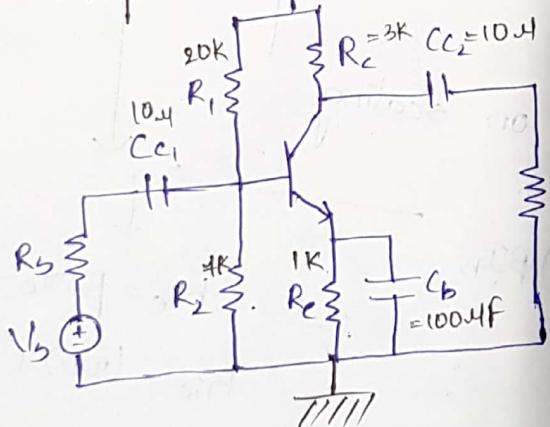

Observing at  
low frequencies  
so  $h$ -parameter  
model.


for Gain - 150 Design ce amplifier, calculate

$R_1, R_2, R_E, R_C$

\* AC Analysis


using linear mode (h-parameter model)

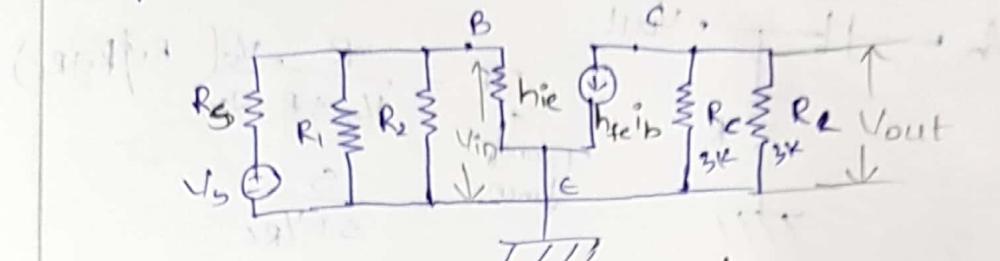1. Ground the DC sources
2. Short circuit all capacitors
3. Replace BJT with h-parameter model



AC equivalent circuit.

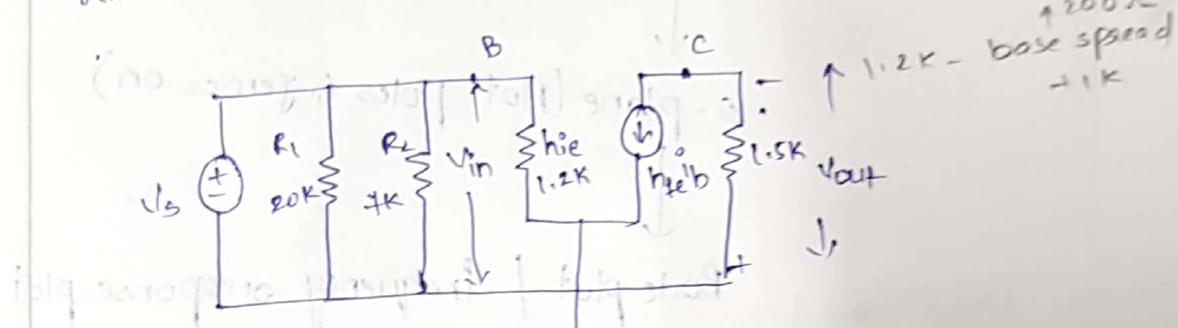When  $R_b = 0$ ,  $V_b$  will appear at  $h_{ie}$  (all are parallel)




$$\text{Gain} = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{(h_{fe}/b) \times 1.5}{h_{ie} \times 1.2}$$

$$150 = \frac{1 - h_{fe}/15}{12} = -\frac{(B) \times 15}{12}$$


$$\text{Actual Gain} = -\frac{100 \times 15}{12} = -125$$

$$\text{Gain at } 10^6 = 20 \log (-125)$$

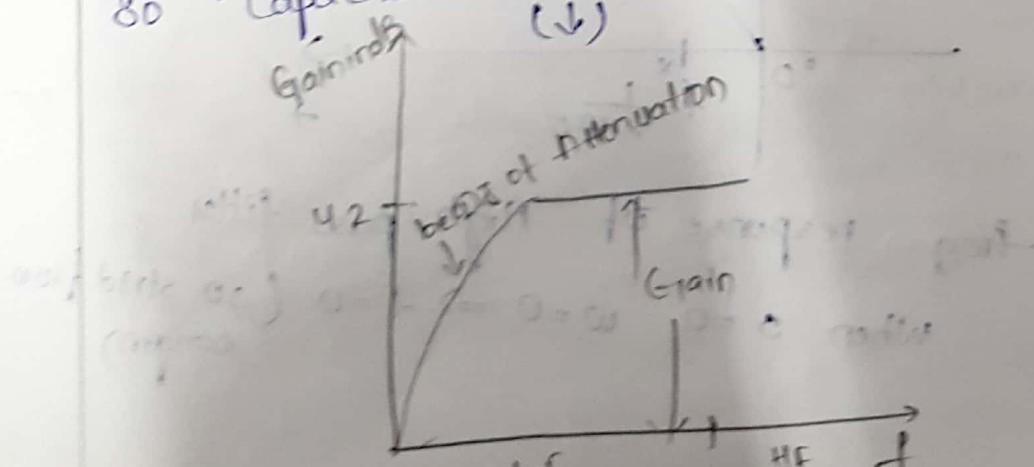As the Gain is  $u_2$ , but at low freq. Gain is falling off bcoz of Attenuation (due to capacitors)  
Capacitors attenuate at low frequencies



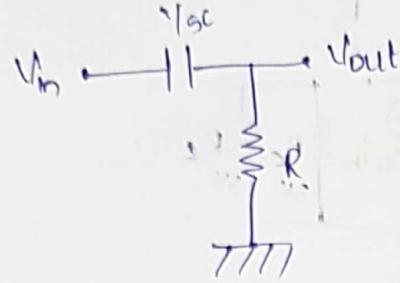\* SYSTEM: deviation around zero pole  $-420 \text{ dB/decade}$   
 consider High pass filter. pole.  $-20 \text{ dB}$



$$\text{TF} = \frac{V_{out}}{V_{in}} = \frac{R}{1/R + R_s} = \frac{R}{1/R + sC} = \frac{sC}{sC + 1/R}$$


Transfer function

(Notes) Transfer funn / Gain


$\downarrow$   
 : s-plane (plot poles & zeroes on)

$\downarrow$   
 Bode plot / frequency response plot

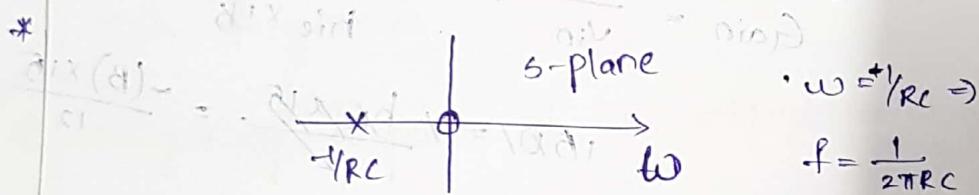\*  $s=0$  is zero &  $s=\frac{1}{RC}$  is pole.



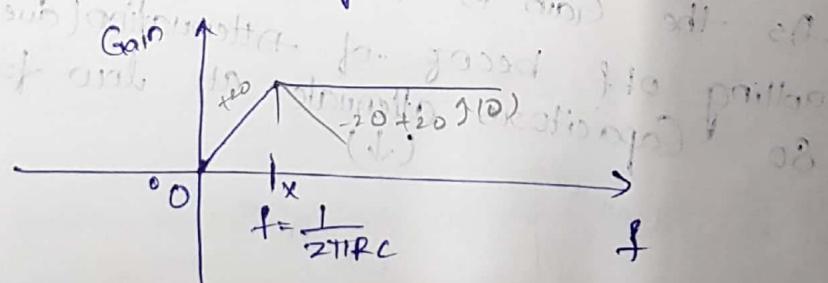
\* When we get a pole the curve deviates around by  $-20 \text{ dB/decade}$  (if it is a zero it deviates by  $+20 \text{ dB/decade}$ )



Freq. response of High pass filter.

When  $s=0 \quad \omega=0 \Rightarrow f=0$  (so start from origin)

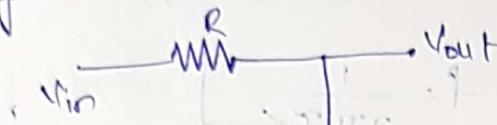\* Low pass filter  
for each RC network it has Time const.  
which generates pole ( $R & C$ ) which affects the gain.



$$\text{Gain} = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{1/C}{R + 1/C} = \left( \frac{1}{s + 1/\text{RC}} \right) \left( \frac{1}{RC} \right)$$


(approx. formula to calculate cut-off freq.)

Transfer funcn / Gain

$$s = \frac{1}{RC} \text{ rad/s}$$

$$\omega = \frac{1}{RC} \text{ rad/s} = \frac{1}{2\pi f} \text{ rad/s}$$

$$f = \frac{1}{2\pi RC}$$

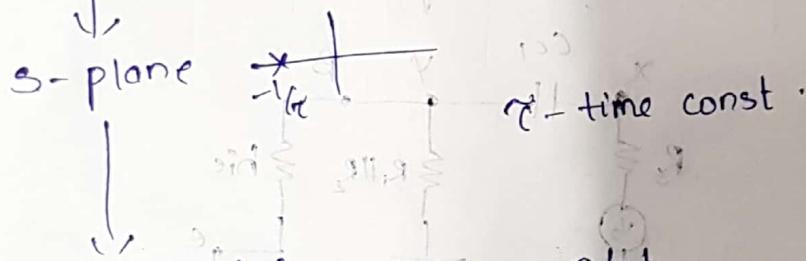


Bode plot / freq. response plot

$$\text{Gain} = \frac{1}{RC} \left( \frac{1}{s + 1/\text{RC}} \right)$$

when  $f = 0 \Rightarrow s = 0$  so Gain = 1

is done

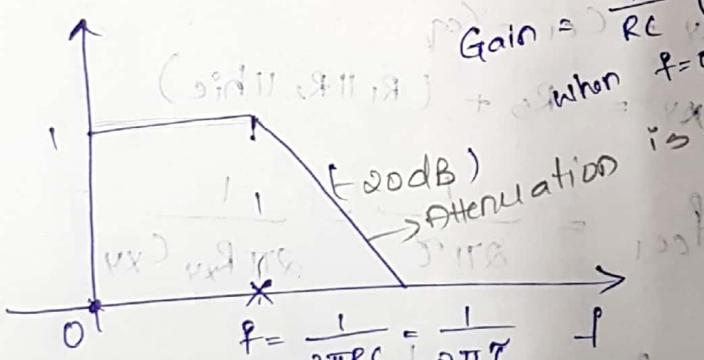

$\gamma$  decides cut off freq


where deviation occurs

→ When we calculate 3 time const.  $\tau_{CC1}$ ,  $\tau_{CC2}$ ,  $\tau_{CB}$  so that we can obtain cut off frequencies from where we can observe the deviations.

3/18/08

3/18/08 - 21 = 1327


3/18/08

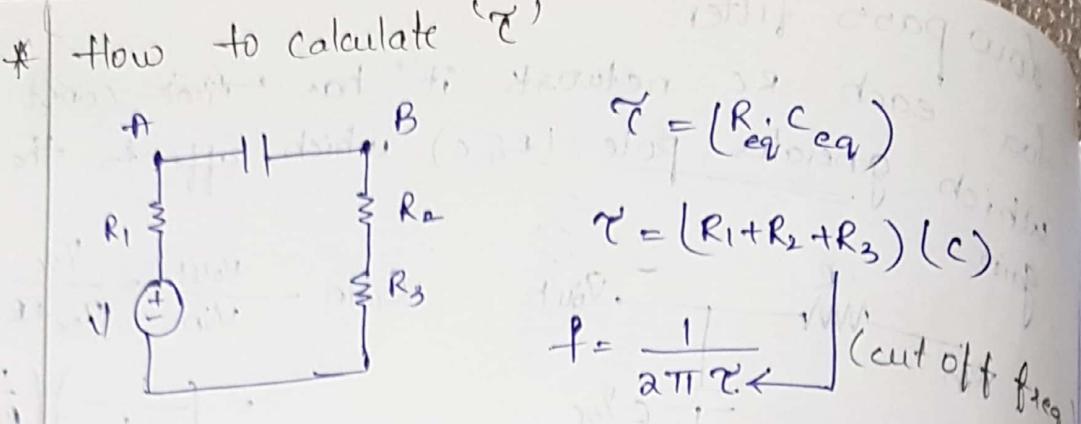

To find effective resistance deactivate the sources (Voltage - short & current - open)

\* Effect of Coupling capacitors & bypass capacitors on frequency response

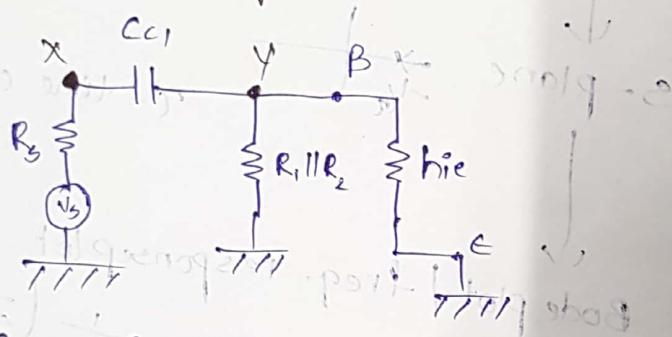1. Effect of coupling capacitor  $C_{c1}$  on freq. response



$$R_{xy} = C_{c1} \omega_{eq}$$

$$R_{xy} = R_s + (R_1 \parallel R_2 \parallel hie)$$

$$f_{cc1} = \frac{1}{2\pi R_{xy} C_{xy}} = \frac{1}{2\pi R_s C_{c1}}$$

$$f_{cc1} = \frac{1}{2\pi C_{c1} (R_s + R_1 \parallel R_2 \parallel hie)}$$

When,  $R_s = 0$

$$f_{cc1} = \frac{1}{2\pi C_{c1} (0.0K \parallel 7K \parallel 1.2K)} \\ = \frac{1}{(2\pi)(10 \times 10^{-6})(974.65)}$$


$$f_{cc1} = 16.329 \text{ Hz}$$

When  $R_s = 1 \text{ k}\Omega$

$$f_{cc1} = \frac{1}{2\pi C_{c1} (1.974 \text{ k}\Omega)}$$



$$= \frac{10^5}{2\pi (1.974 \times 10^3)} \\ = 8.06 \text{ Hz} \\ \approx 8 \text{ Hz}$$

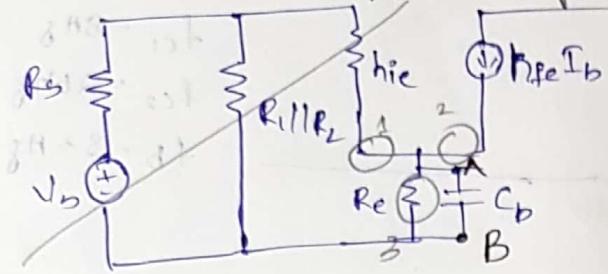2. Effect of bypass capacitor ( $C_b$ ) on  $f_{eq}$ . response.



$$R_T = (R_1 \parallel R_2 \parallel R_e) + h_{ie}$$

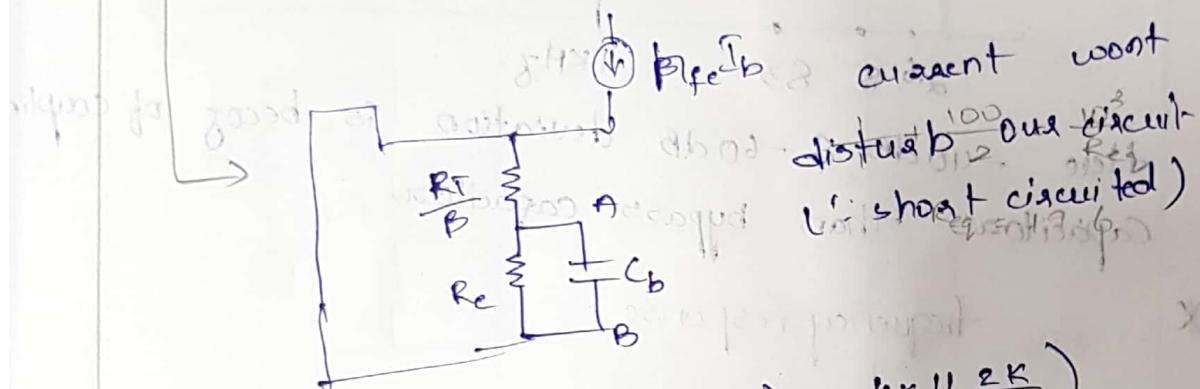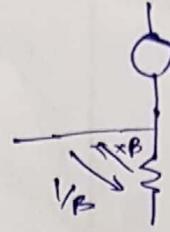
$$R_T = (1.2K \parallel 20K \parallel 1K) + 1.2K \\ = 2K$$



$$R_{eq} = R_{AB} = \left( R_e \parallel \frac{R_T}{P} \right) = \left( 1K \parallel \frac{2K}{100} \right) \\ = 19.6\Omega$$

$$f_{eq} = \frac{1}{2\pi R_{eq} C_{eq}} = \frac{1}{2\pi \times 19.6 \times 10^{-6} \times 19.6} \\ = 83 \text{ Hz}$$

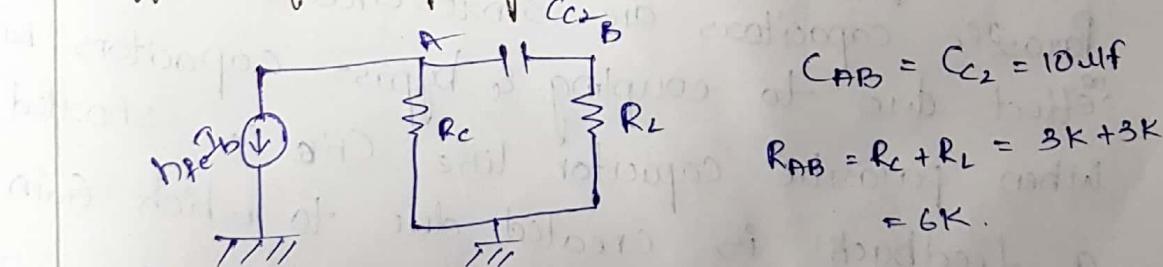3. Effect of coupling capacitor ( $C_{C2}$ ) on  $f_{eq}$ . response




$$C_{AB} = C_{C2} = 10\text{nF}$$

$$R_{AB} = R_C + R_L = 3K + 3K \\ = 6K$$

$$f_{CC2} = \frac{1}{2\pi C_{C2} \times R_{AB}} = \frac{1}{2\pi \times 10\text{nF} \times 6K} = \frac{1}{(10\text{nF})(6K)}$$

$$f_{CC2} = 2.6 \text{ Hz}$$

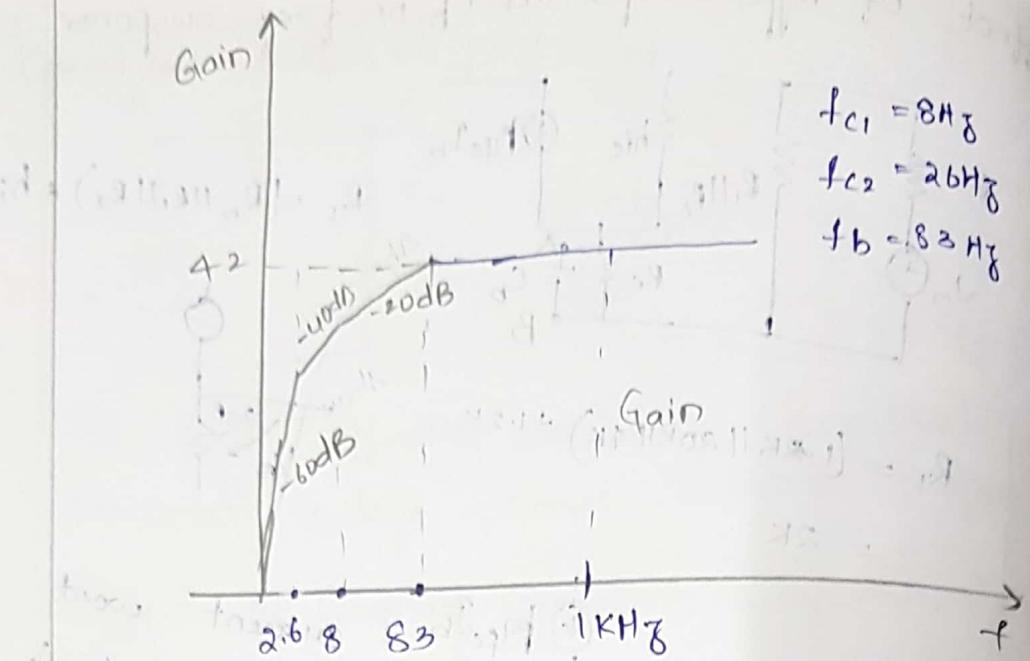\* Coupling & bypass capacitors effect freq. response at low frequencies.



$$f_{C1} = 8 \text{ Hz}$$

$$f_{C2} = 26 \text{ Hz}$$

$$f_b = 83 \text{ Hz}$$

Here  $-40 \text{ dB}$  &  $-60 \text{ dB}$  deviation is bcoz of cap. Capacitors than bypass capacitors.





frequency response

$$\frac{V_o}{V_s} = \frac{(1 + A_f)}{1 + A_f + 1/A_s}$$

w.r.t  $A_f$  :  $\frac{V_o}{V_s}$  = w.r.t  $A_f$  =  $\alpha$

- \* frequency response of BJT Amplifier at High frequency
- effect of Parasitic Capacitances on frequency response  
Generally we have two capacitances - extra diffusion & transition capacitances (Parasitic Capacitances)  
For high frequencies all capacitors including parasitic capacitors are short circuited. So there is no effect due to coupling & bypass capacitors but when parasitic capacitor like  $C_{bb'}$  is shorted a feedback is created due to which Gain falls. So there is a roll off at high frequencies also. So as Gain  $\downarrow$  the Gain & frequency graph is drawn.
- Here we replace BJT / Transistor with  $\pi$ -model (In General we place 2 capacitors in h-parameter, so that it can resemble to  $\pi$ -model)

# AC Analysis

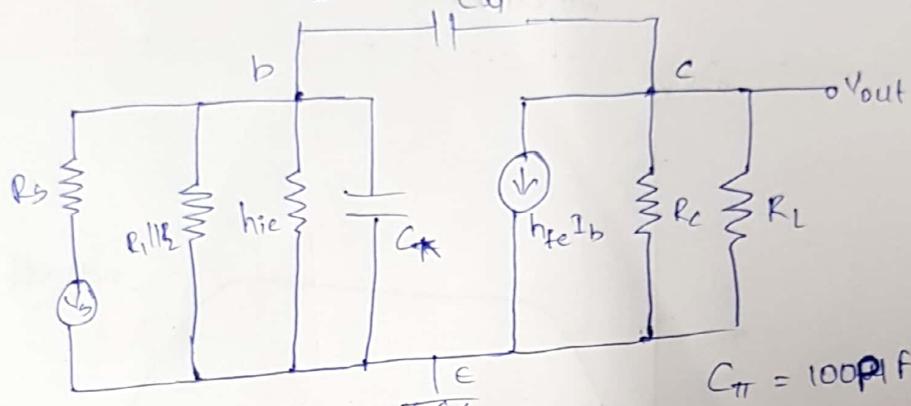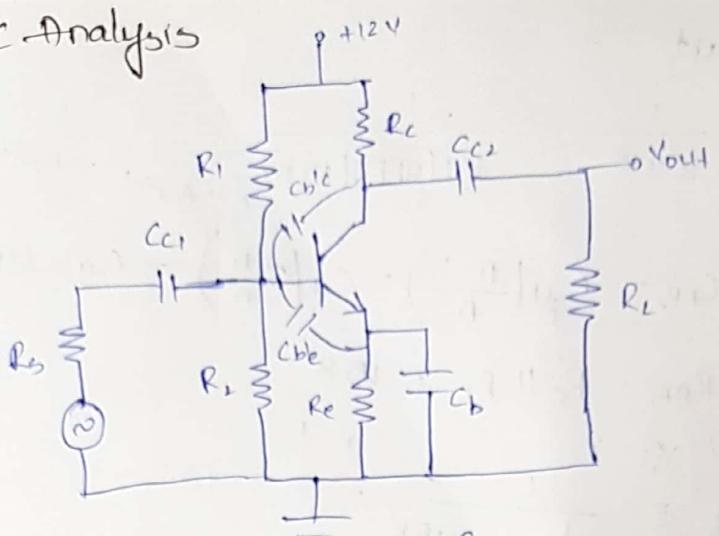


AC equivalent circuit

$$C_{pi} = 100 \text{ pF}$$

$$C_{pi} = 4 \text{ pF}$$

Here, analysis of about circuit becomes complex as  $C_{pi}$  is connected across i/p & o/p so to make it simple we modify the circuit according

to Millers theorem.

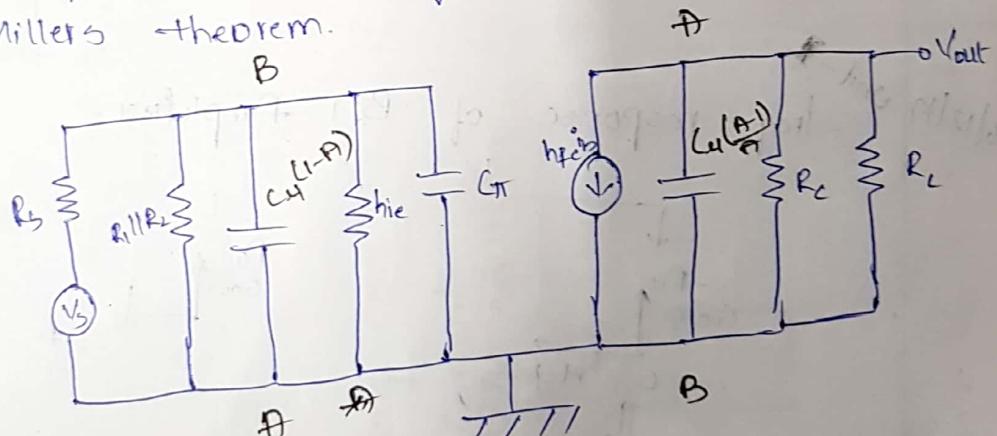

We analyse i/p side & o/p side.

At i/p

$$f_{in} = \frac{1}{2\pi R C} = \frac{1}{2\pi R_{eq} C_{eq}}$$

$$C_{eq} = C_{AB} = C_{pi}(1-A) + C_{pi}$$

$$R_{eq} = R_{AB} = R_s || R_1 || R_2 || h_{ie}$$

$$f_{in} = \frac{1}{2\pi (R_s || R_1 || R_2 || h_{ie})(C_{pi}(1-A) + C_{pi})}$$


At output

$$I_{out} = \frac{1}{2\pi R} = \frac{1}{2\pi(4PF)(15k)} \quad (\because A_v \gg 1 \therefore A_v \approx A)$$

$$C_{eq} = C_{AB} = C_A \left( \frac{n-1}{n} \right) = C_A \left( \frac{n-n}{n} \right) = C_A = 4PF$$

$$R_{eq} = R_{AB} = R_C \parallel R_L = 15k$$
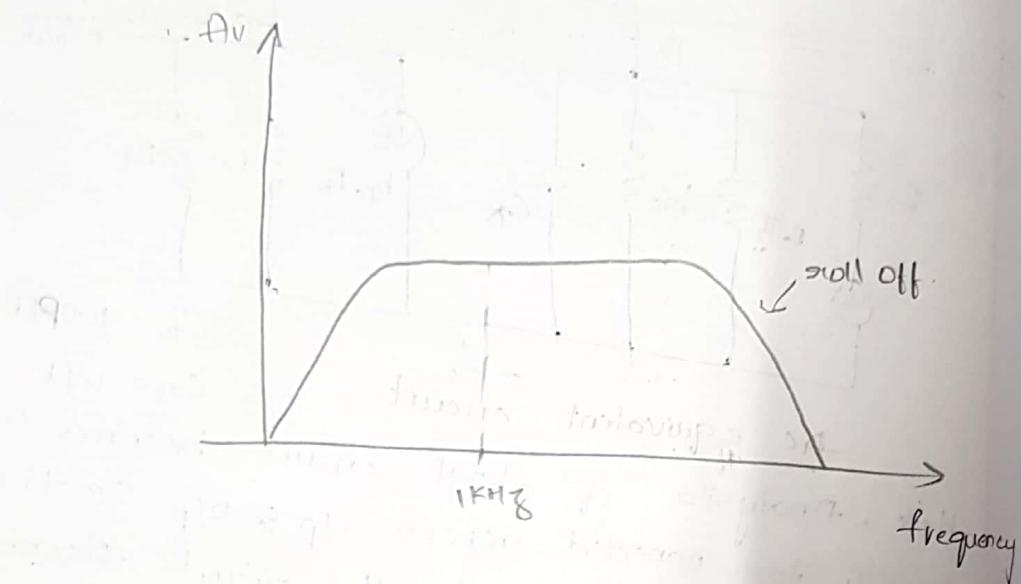
$$I_{out} = \frac{1}{2\pi \times 4PF \times 15k}$$



16/12/19

Unit - freq. response of BJT Amplifier.



Low freq. response  $\rightarrow$  1. Effect of bypass/coupling capacitors on freq. response

High freq. response  $\rightarrow$  2. Effect of parasitic capacitance on freq. response

$\pi$  model

$$\tau_{bb} = h_{ie} + \tau_B \quad | \quad h_{par} = \frac{h_{fe}}{g_m} \quad | \quad \pi \text{ model}$$


$$\tau_{bb} = h_{ie} + \tau_B$$

$$= \frac{h_{fe}}{g_m}$$

$$\alpha / r_e$$


$$h_{fe} / r_{in}$$

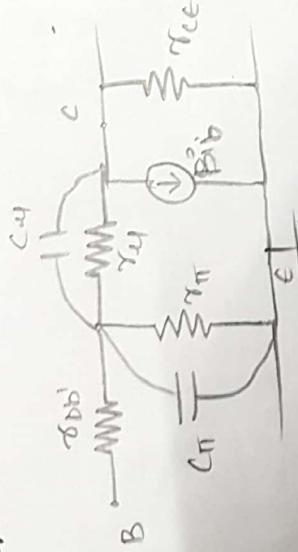Hybrid  $\pi$ -model:  
Current control - current source




How dP current changes w.r.t  $B$   
decided by factor  $B$

Voltage control - voltage source

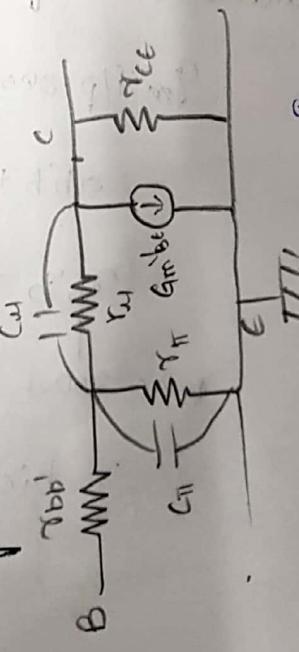


$G_m$  - Trans conductance =  $\frac{I_c}{V_{BE}}$   
How dP current changes w.r.t  $V_{BE}$  is decided  
by factor  $G_m$


$h$ -parameter (approx)

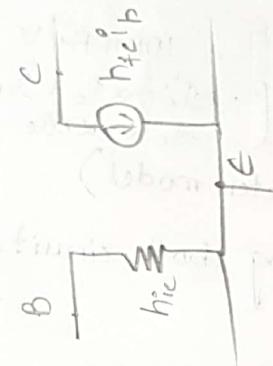

$\pi$  model

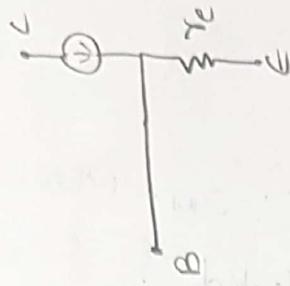

We use Voltage controlled current source

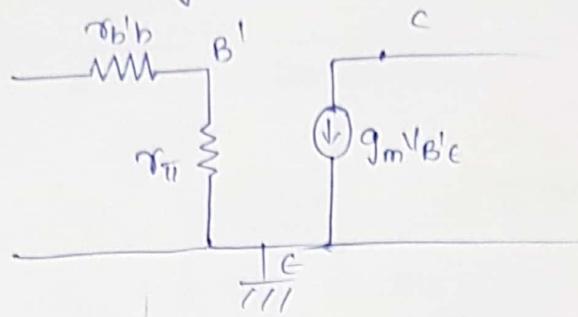

We neglect  $r_{pi}$ ,  $C_{pi}$ ,  $C_{pi}$  ( $\because C_{pi} = M \approx 0$ )  
 $C_{pi}$  &  $C_{pi}$  - PF storage (neglected.)

Calculation of  $g_m$  ( $r_e$ )

$$g_m = \frac{\partial I_c}{\partial V_{BE}} = \alpha \left( \frac{\partial I_c}{\partial V_{B'E}} \right) = \frac{\alpha}{r_e} = \frac{1}{10} = < 0.1$$

$$g_m = \frac{I_c}{V_{BE}} \quad B = \frac{I_c}{I_B} \quad \left( \begin{array}{l} \because I_c = \alpha I_e + I_{CEO} \\ \frac{\partial I_c}{\partial I_e} = \alpha \end{array} \right)$$

Calculation of  $g_m$  (h-parameter model)

$$g_m v_{BE} = h_{fe} i_b \quad (\text{comparing both circuits})$$

$$g_m = \frac{h_{fe} i_b}{v_{BE}}$$

$$g_m = \frac{(h_{fe})}{r_{pi}} = 100 \text{ mA/V}$$

Calculation of  $g_m$  ( $K$ )  $\sigma_{b'b}(h)$

$g_m$  i/p resistance of  $\pi =$  i/p of  $h$

$$\sigma_{b'b} + \sigma_{pi} = h_{ie}$$

$$\sigma_{b'b} = h_{ie} - \sigma_{pi}$$

Take  $200\Omega$   $\therefore 1K$ .

$$\therefore h_{ie} = 1.2K\parallel$$

# Calculation of $\gamma_{\pi}$


$$\text{WKT, } g_m = \frac{h_{fe}}{\gamma_{\pi}}$$

$$\therefore \gamma_{\pi} = \frac{h_{fe}}{g_m} = \frac{100}{100 \text{ mA/V}} \Rightarrow \gamma_{\pi} = 1 \text{ K.N}$$


Current Gain ( $R_L = 0$ ) / ( $R_L + 0$ )

Case (i) :  $R_L = 0$  (short circuit current gain)

Consider only transistor circuit

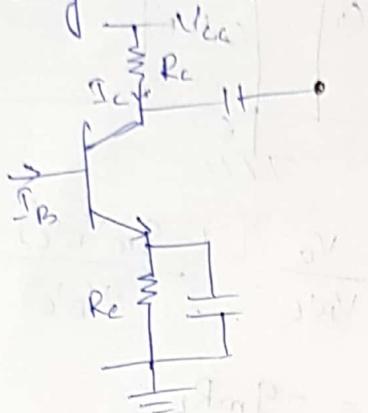

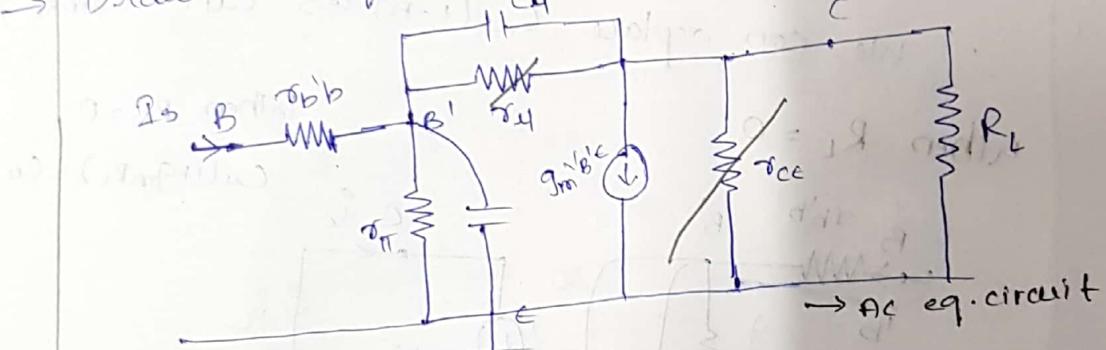→ Draw AC equivalent circuit for analysis.




Approximations  
 $r_{ce}$  &  $r_{pi}$  are neglected as their values are

very - very large


We have to find short circuit current since  
 $R_L = 0$

After Approximation,

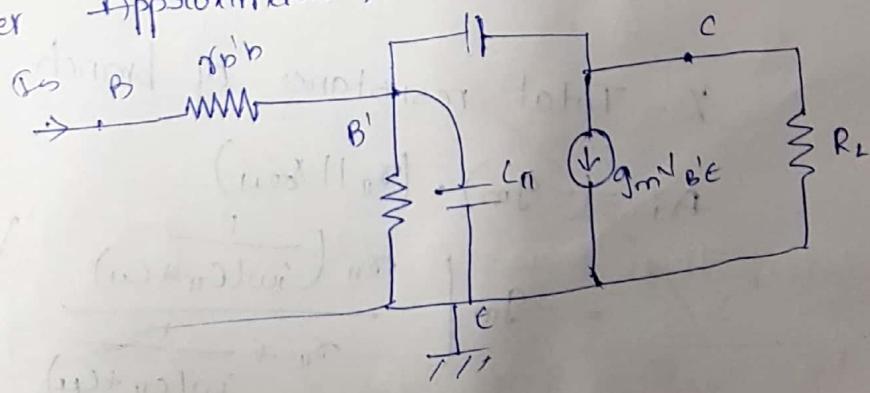

We have branch capacitors ( $C_{\text{u}}$ ) so it's easy

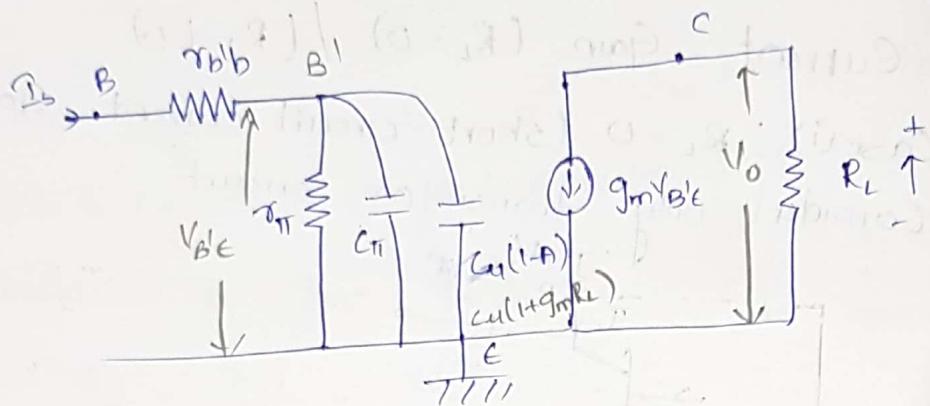Analysis We can connect them on i/p. side & o/p side by using miller's theorem as  $C_{\text{u}}(1-A)$ ;  $(C_{\text{u}} \left( \frac{A-1}{A} \right) \approx C_{\text{u}})$  ( $\because A$  is voltage gain  $>> 1$ )  $C_{\text{u}}$  is neglected ('very small')



$$A = A_V = \frac{V_O}{V_{B'E}} = \frac{(-g_m V_{B'E}) R_L}{V_{B'E}} = -g_m R_L$$


$$\therefore A = -g_m R_L$$

$\therefore$  We can replace  $C_{\text{u}}(1-A)$  as  $C_{\text{u}}(1+g_m R_L)$

When  $R_L = 0$

When  $R_L = 0$
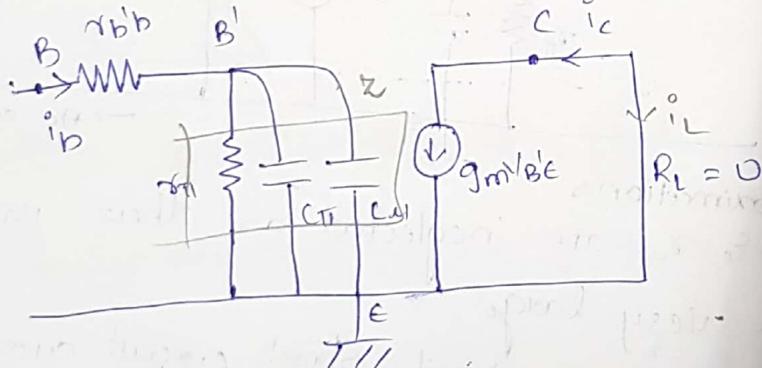
$$C_{\text{u}}(1+g_m R_L) = C_{\text{u}}$$



$$A_i = \frac{i_L}{i_B} = \frac{\frac{-i_o}{z}}{\frac{i_b}{z}} = \frac{g_m V_{B'E}}{(V_{B'E}/z)} = (-g_m z)$$

$z$  - Total resistance of branch

$$A_i = (-g_m) \cdot (\frac{1}{r_{\pi}} || \frac{1}{r_{\pi u}})$$

$$= -g_m \left( \frac{\frac{1}{j\omega(C_{\pi} + C_{\text{u}})}}{\frac{1}{r_{\pi}} + \frac{1}{j\omega(C_{\pi} + C_{\text{u}})}} \right)$$

$$A_i = \left[ \frac{-g_m \gamma_{\pi}}{1 + j \omega \gamma_{\pi} (C_{\pi} + C_{\mu})} \right]$$

$$= \left| \frac{g_m \gamma_{\pi}}{1 + j \omega \gamma_{\pi} (C_{\pi} + C_{\mu})} \right|$$

→  $\gamma$  for the circuit,

$$\gamma = R_{eq} \times C_{eq} = \gamma_{\pi} (C_{\pi} + C_{\mu})$$

$$f_c = \frac{1}{2\pi \gamma} = \frac{1}{2\pi \gamma_{\pi} (C_{\pi} + C_{\mu})} = f_B$$


$\uparrow$  cut off freq. We can neglect  $C_{\mu}$  as it is small but too consider for notation

$$A_i = \frac{h_{fe}}{1 + j(f/f_B)}$$

$$A_i = \left| \frac{h_{fe}}{1 + j(f/f_B)} \right|$$

$$= \frac{h_{fe}}{\sqrt{(1 + (f/f_B)^2)}}$$

freq. response plot ( $A_i$ )

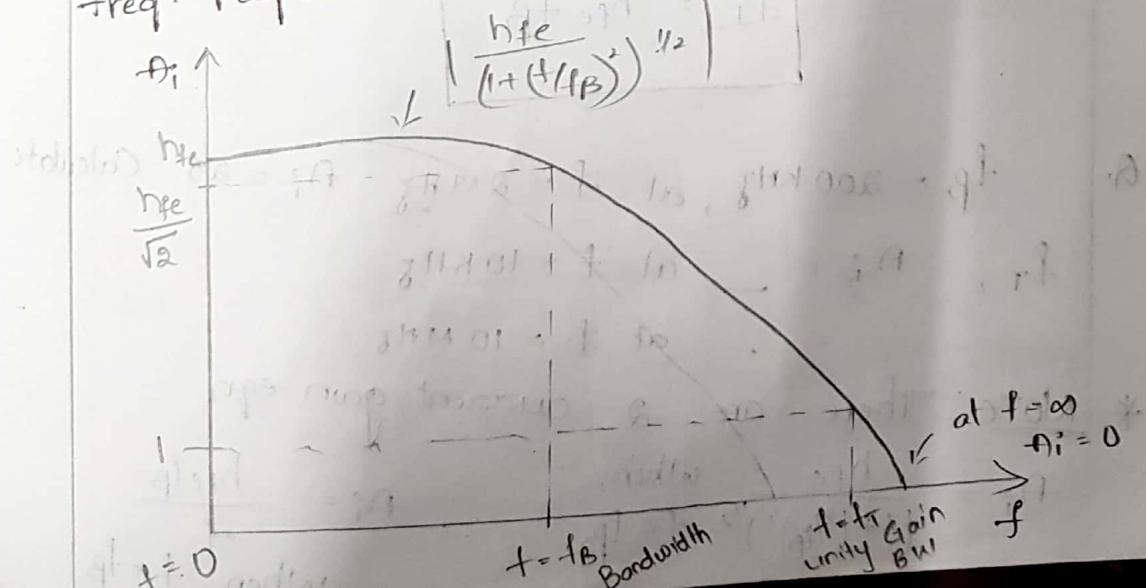

We have,

$$A_i = \left| \frac{h_{fe}}{\left(1 + \left(\frac{f}{f_B}\right)^2\right)^{1/2}} \right|$$

(i)  $\left(A_i\right)_{f=0} = h_{fe}$

(ii)  $\left(A_i\right)_{f=f_B} = \frac{h_{fe}}{\left(1 + \left(\frac{f_B}{f_B}\right)^2\right)^{1/2}} = \frac{h_{fe}}{\sqrt{2}}$   $f_B$ -cut off freq.  
where gain

(iii)  $\left(A_i\right)_{f=f_T} = \frac{h_{fe}}{\left(1 + \left(\frac{f_T}{f_B}\right)^2\right)^{1/2}}$  roll off by  $\frac{1}{2}$   
max. value

But from graph,

$f_B$  is  $\frac{1}{2}$  cut off freq. &  $f_T \gg f_B$

$$\frac{f_T}{f_B} \gg 1$$

$$\therefore \left(A_i\right)_{f=f_T} = \frac{h_{fe}}{\left(\frac{f_T}{f_B}\right)^2}^{1/2} = \frac{h_{fe} f_B}{f_T}$$

But at  $f=f_T$ ,

$$A_i = 1$$

$$\frac{h_{fe} f_B}{f_T} = 1$$

$$\therefore f_T = h_{fe} f_B$$

Q.  $f_B = 200 \text{ kHz}$ , at  $f = 2 \text{ MHz}$   $A_i = 25$ . Calculate


$f_T$ ,  $A_i =$  \_\_\_\_\_ at  $f = 10 \text{ kHz}$

\_\_\_\_\_ at  $f = 10 \text{ MHz}$

\* Note: There are 2 current gain eqn

$$A_i = \frac{h_{fe}}{\left(1 + \left(\frac{f}{f_B}\right)^2\right)^{1/2}} \text{ when, } f < f_B$$
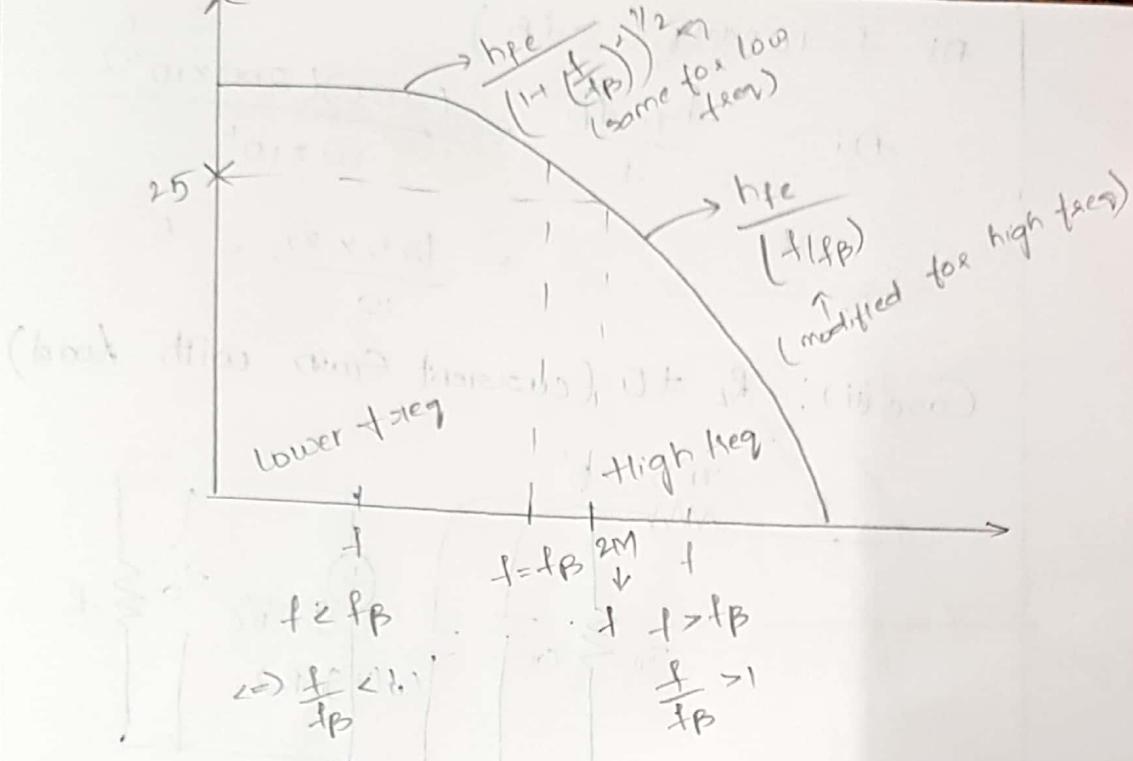
$$A_i = \frac{h_{fe} f_B}{f} \text{ when, } f > f_B$$



Given, at  $f = 2 \text{ MHz}$   $A_i^o = 25$

But  $f$  is high freq ( $f > f_B$ )

$$A_i = \frac{h_{fe}}{1 + f/f_B}$$

$$\Rightarrow \frac{25 \times 2 \times 10^6}{200 \times 10^3} = h_{fe}$$

$$(25 h_{fe}) = 250$$

When,  $f = f_T$   $A_i^o = 1$

(At  $A_i = 1$ ,  $f_T > f_B$  we have,  $A_i = \frac{h_{fe} f_B}{f_T}$ )

$$1 = \frac{(250)(200 \times 10^3)}{f_T}$$

$$f_T = 50 \text{ MHz}$$


At  $f = 10 \text{ kHz}$  ( $< f_B (200 \text{ kHz})$ )

$$A_i = \frac{h_{fe}}{\left[1 + \left(\frac{f}{f_B}\right)^2\right]^{1/2}} = \frac{250}{\left[1 + \left(\frac{10 \times 10^3}{200 \times 10^3}\right)^2\right]^{1/2}} = 249.68$$

At  $f = 10 \text{ MHz} (> f_B)$

$$A_i = \frac{h_{fe} f_B}{f} = \frac{(250)(200 \times 10^3)}{10 \times 10^6}$$
$$= \frac{(25 \times 2)}{10} = 5$$

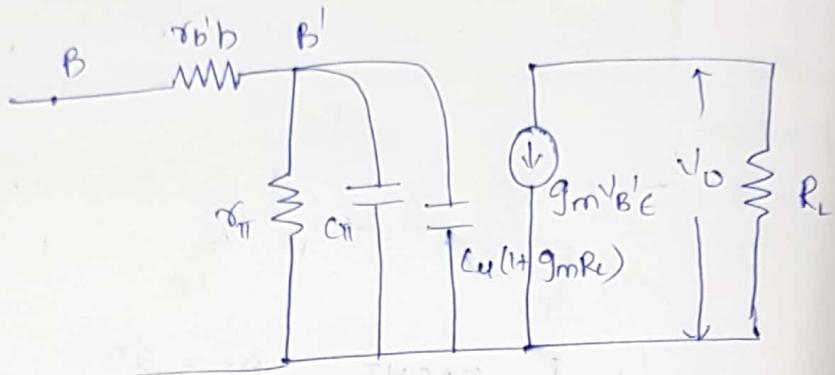Case (ii):  $R_L \neq 0$  (sufficient gain with load)



$$A_i = \left| \frac{V_o}{I_{in}} \right| = \frac{-g_m V_{B'E}}{\sqrt{B'E} / 2} = -g_m Z$$

$$\left| \frac{-g_m \cdot \pi_T}{(1 + j 2\pi f (\pi_T) (C_T + C_4 (1 + g_m R_L)))} \right|$$

$$\propto \rightarrow \pi_T \parallel C_T + C_4 (1 + g_m R_L)$$


for cut off frequency,  $\omega_c = f_c$

$$\omega_c = \text{Req} C_{eq} = \pi_T (C_T + C_4 (1 + g_m R_L))$$

$$f_c = \frac{1}{2\pi (C_T + C_4 (1 + g_m R_L))} = f_B$$

$$\therefore A_i = \left| \frac{h_{fe}}{1 + j (f/f_B)} \right|$$

$$A_i = \left| \frac{h_{fe}}{(1 + (f/f_B)^2)^{1/2}} \right|$$

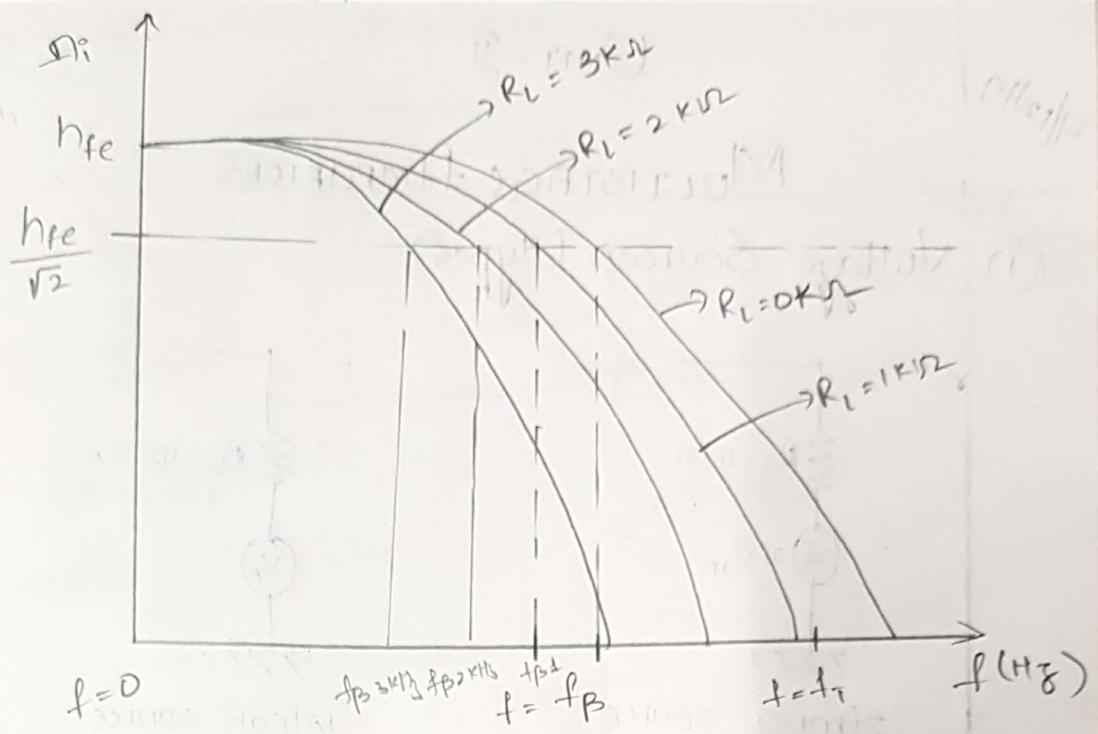

WKT,

$$f_B = \frac{1}{2\pi(\omega_0)(C_n + C_{ul}(1+g_m R_L))}$$

$$f_B \propto \frac{1}{1 + g_m R_L} \quad \therefore \text{roll off depends on } f_B$$

As \$R\_L \uparrow \quad f\_B \downarrow \quad \begin{matrix} \text{upper cut off freq} \\ \downarrow \quad \uparrow \end{matrix} \quad \begin{matrix} \text{lower cut off freq} \\ \downarrow \quad \uparrow \end{matrix} \quad (f\_B - 0 = f\_B) \text{ also } 0

When \$f\_B \downarrow \quad \text{Bandwidth } (f\_B - 0) = f\_B\$ also 0

Effect of bypass coupling & problem  
at high freq. response / low freq. response  
 $\omega_i - R_L = 0$

(except) distortion x.  
with gm & op. point

points

1) \$f\_B\$ is the cutoff freq. of the circuit & \$f\_B^2\$

2) losses due to \$(gm)^2\$ of bypass

3) due to load on output port & its effect on gain